

If the grid bias on a variable-mu valve is altered by means of a manually operated potentiometer, or is automatically controlled depending on the strength of the alternating input to the valve grid, so either manual or automatic control of the gain of an R.F. amplifier is achieved. This leads to the common forms of manual and automatic volume control methods used in broadcast receivers.

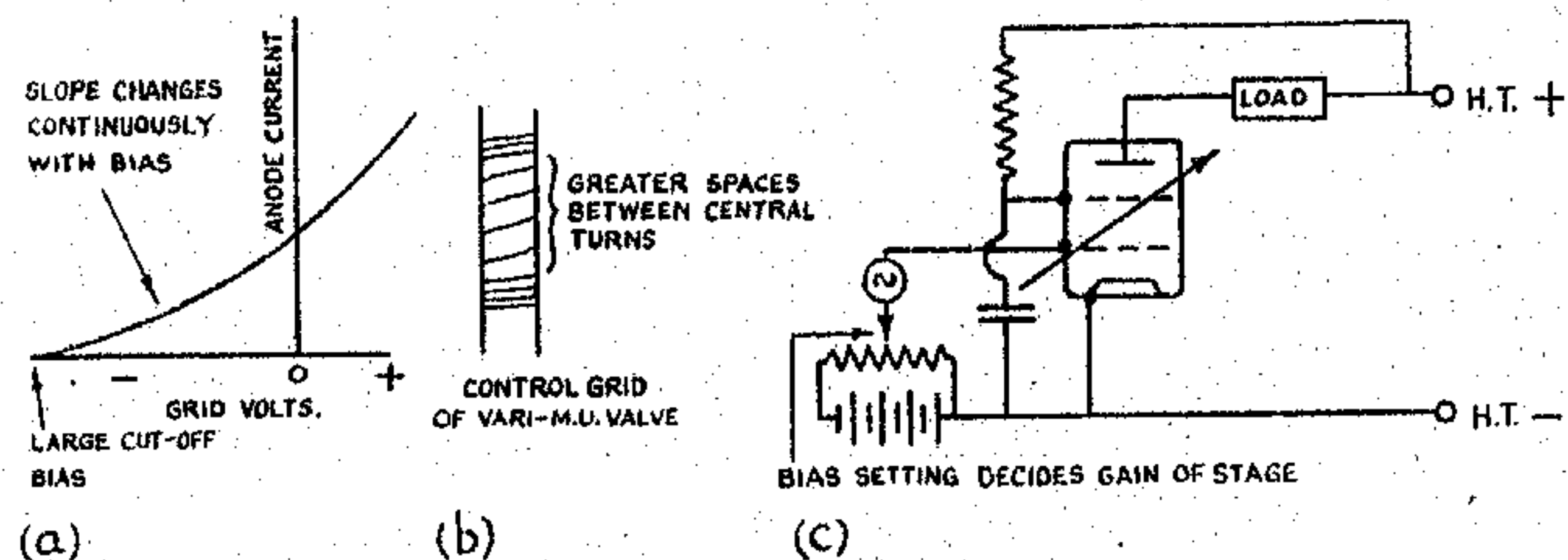


FIG. 61. The Action of the Variable-mu Valve.

Power Amplification. In using a valve as a power amplifier, the aim is to supply maximum power to the anode load with as little distortion as possible, instead of maximum voltage variation across the load. This demands large current variations through the load, so that if the use of excessive voltage variations across the valve is to be avoided, the valve must necessarily have a low A.C. resistance. Hence the power valves used as output valves in receivers, transmitters and other electronic apparatus where electrical power is converted into mechanical power or electromagnetic radiation, have much lower A.C. resistances than the voltage amplifying valves in electronic equipment. The latter usually serve to supply the power valve with a sufficiently large grid swing voltage, demanding little or no power consumption.

Let a valve amplifier be operated so that

E_G = input voltage to grid, R.M.S. value.

μ = amplification factor of valve.

R_A = A.C. resistance of valve.

R_L = anode load resistance.

Assuming the grid is not driven positive, so that grid current is avoided, then the effective anode voltage variation due to an

input of E_G volts is μE_G . The corresponding current I is $\mu E_G / (R_A + R_L)$. The power developed across the anode load is therefore $I^2 R_L = \frac{(\mu E_G)^2 \cdot R_L}{(R_A + R_L)^2} = P$.

This will be a maximum for a value of R_L given by putting $dP/dR_L = 0$.

$$(\mu E_G)^2 \left[\frac{(R_A + R_L)^2 - R_L \cdot 2(R_A + R_L)}{(R_A + R_L)^4} \right] = 0.$$

$$\therefore R_A + R_L - 2R_L = 0.$$

$$\therefore R_A = R_L. \quad (181)$$

As in the case of any other form of electric generator, maximum power is supplied to the load when the load resistance equals the internal resistance of the source of supply. However, the requirement of low distortion must also be fulfilled, requiring extra consideration of the optimum load resistance value to be used.

Class A Power Amplification. The anode load of a power amplifier must necessarily be a resistive device; power cannot be dissipated in the wattless reactive components, condensers and inductances, in which the current differs in phase by 90° from the voltage. The usual loads are therefore ordinary resistances, or resistive elements such as loudspeakers, headphones, electric meters, telephone meters or aerials radiating energy or such resistances coupled to the power valve by a matching transformer or tuned circuits of the rejector circuit type with a make-up current in phase with the applied A.C. voltage: simulating a resistance in their effect. If a resistance is inserted directly in the anode circuit of the valve, then class A amplification conditions must be observed using an ordinary amplifier if distortion is to be avoided. This brings about the limitation that the grid swing voltage is restricted, and also that an increase of anode current brought about by a reduction of negative grid voltage is accompanied by an increase of anode load voltage, with a consequent reduction of anode volts, and hence power output.

Suppose a power valve has constants μ , g_m and R_A , and it operates with a mean, steady anode voltage V_A . Let $-V_G$ be the cut-off grid bias with this anode voltage. An alternating grid voltage is applied which, at its positive peak value, just brings the grid potential to zero, whereas at the negative peak value the

The power output at this optimum load value will be

$$P = \frac{\mu^2 V_G^2 R}{2(R+2R_A)^2} = \frac{V_A^2 \cdot 2R_A}{32R_A^2} = \frac{V_A^2}{16R_A}$$

The Load Line. The selection of an anode load of value $R=2R_A$ leads theoretically to the attainment of maximum undistorted power output from a power valve. Though serving as a useful guide in practice to the choice of load values in the case of triodes, yet a more accurate assessment of the load is required if distortion is to be kept to a minimum, since allowance must be made for the departure from linearity of the valve characteristics when operating near anode current cut-off. Moreover, using pentode power valves, the selection of a load $R=2R_A$ gives far from satisfactory results. The approach adopted is to draw a load line, which is a line representing the voltage-current characteristic of the anode load, superimposed on the anode voltage-anode current characteristics for the valve in question. If the anode load is a resistance then, by Ohm's law, the load line is straight. For an impedance as anode load which is sensibly reactive in its effect, the load line will be an ellipse.

In general, two methods of approach are used. Either the load resistance value is known, and it is required to estimate the percentage harmonic distortion if the valve operating conditions are also specified, or alternatively, a certain power valve is to be used, and the graphical method outlined below is adopted as a means of estimating the best operating potentials for the valve, and the best load resistance value to use in order to keep the distortion satisfactorily low.

Suppose a triode power valve with a total H.T. supply of 400 V. is used. A limitation to the total power which can be dissipated is set by the maximum temperature at which the anode can be safely operated. Let this correspond to 16 W. maximum anode dissipation. The static anode voltage : anode current curves are known, as in fig. 62. The curve representing 16 W. dissipation is drawn on these characteristics by plotting $V_A I_A = \text{constant}, 16$. When the anode current is zero (obtained in practice by setting the grid bias at cut-off), the voltage drop in the anode load is zero so the anode will be at the full H.T. voltage, 400. Hence the point A where $V_A=400, I_A=0$ is one point on the required load line. If class A conditions are to be observed, the peak positive

dynamic characteristic ($I_A - V_G$) of the valve just begins to bend, so that class A conditions are observed (cf. p. 119). Let $2I_A$ be the total peak-to-peak anode current excursion brought about by the maximum permissible grid voltage change. Then the anode potential will be caused to vary from $V_A + I_A R$ to $V_A - I_A R$, if R is the resistive anode load. A change of anode potential of $I_A R$ is compensated by a change of grid voltage of $I_A R / \mu$, so that when the anode potential is a maximum at $(V_A + I_A R)$, the necessary cut-off bias will be $[-V_G - (I_A R / \mu)]$. Assuming the valve $I_A - V_G$ characteristic is linear down to the cut-off bias value, then the maximum permissible peak grid voltage input is $\frac{1}{2}[V_G + (I_A R / \mu)]$.

But $I_A = \frac{\mu E_G}{R + R_A}$, and substituting for E_G

$$I_A = \frac{\mu}{R + R_A} \cdot \frac{1}{2} \cdot \left(V_G + \frac{I_A R}{\mu} \right)$$

$$\therefore I_A \left\{ 1 - \frac{R}{2(R + R_A)} \right\} = \frac{\mu V_G}{2(R + R_A)}$$

$$\therefore I_A (2R_A + R) = \mu V_G$$

$$\therefore I_A = \frac{\mu V_G}{R + 2R_A}$$

The power output P will be $I_{R.M.S.}^2 R$, where $I_{R.M.S.} = I_A / \sqrt{2}$.

$$\therefore P = \frac{\mu^2 V_G^2 R}{2(R + 2R_A)^2}$$

To find the value of the anode load R at which this power output is a maximum, put $dP/dR = 0$.

$$\therefore \frac{\mu^2 V_G^2}{2} \cdot \frac{d}{dR} \left\{ \frac{R}{(R + 2R_A)^2} \right\} = 0$$

$$\therefore (R + 2R_A)^2 - R \cdot 2(R + 2R_A) = 0$$

$$\therefore R^2 + 4RR_A + 4R_A^2 - 2R^2 - 4RR_A = 0$$

$$\therefore 4R_A^2 = R^2$$

$$\therefore R = \pm 2R_A \quad (182)$$

So the maximum power output is obtained when the anode load is twice the A.C. resistance of the valve.

grid input voltage just makes the grid potential zero or, at the most, slightly positive. Let B be the point where the zero grid voltage characteristic intersects the maximum dissipation curve. Then AB is the load line for maximum allowable power output. The slope of this load line obtained from $\frac{AC \text{ in volts}}{MC \text{ in amp.}}$ gives the corresponding resistance value to be used.

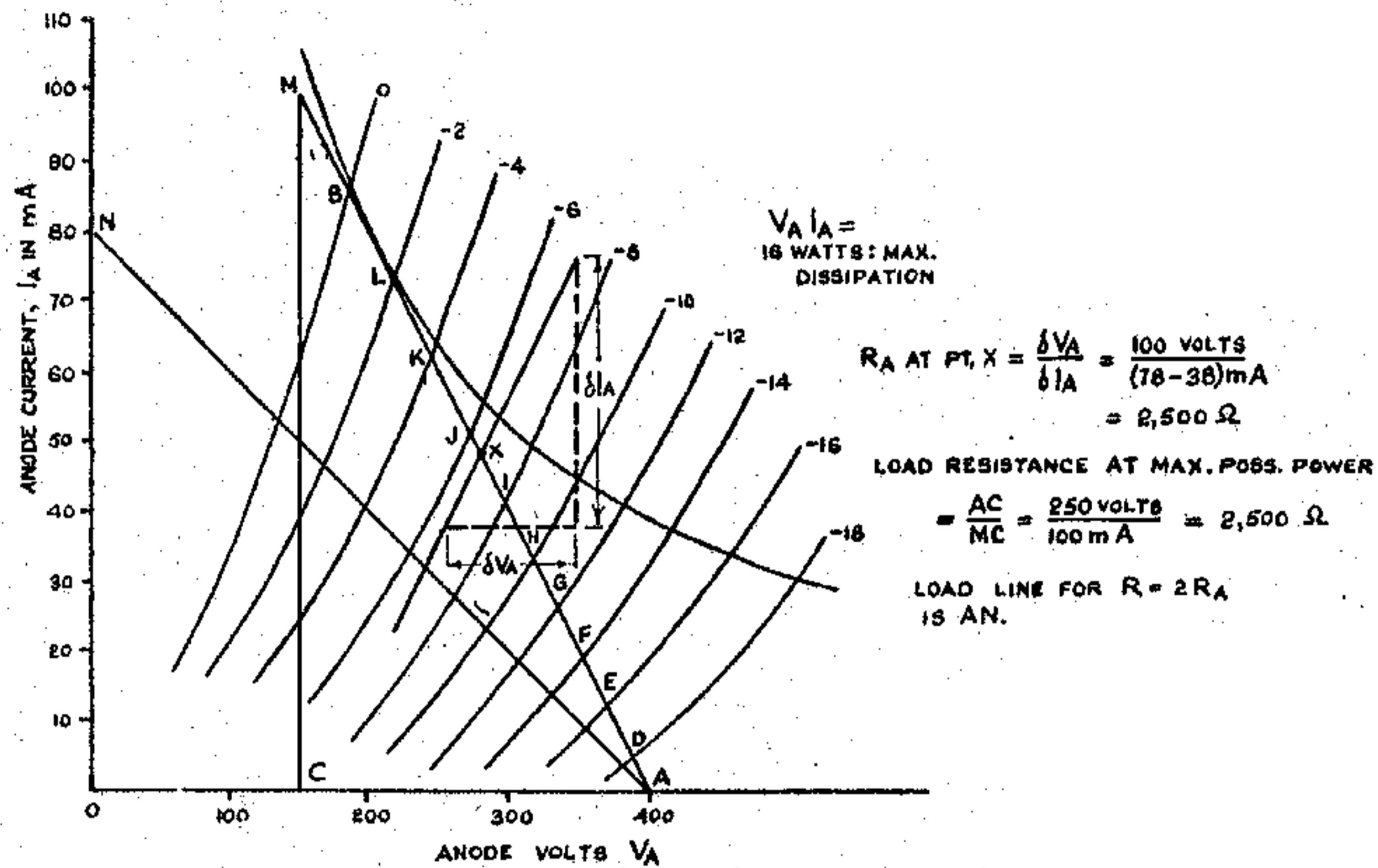


Fig. 62. The Load Line.

What is to be the criterion as regards distortion? Manifestly a small change of grid voltage anywhere in the region from $V_G=0$ to $V_G=\text{cut-off}$ should bring about the same change in current through the anode load irrespective as to whether this grid voltage change takes place near cut-off bias, near the operating bias or near zero. Interpreted graphically, this means that the intercepts cut off along the load line by neighbouring $V_A : I_A$ characteristics should be equal for equal change of grid voltage in moving from one characteristic to the next, i.e. the intercepts $DE, EF, FG, GH, HI, IJ, JK, KL, LB$ (fig. 62) should all be equal. If the load line as drawn does not produce such equal intercepts then it must be varied. Graphically this implies swinging the load line about the fixed point A to arrange it below the line AB so that these intercepts are as nearly equal as possible. At the same time the slope of the line does not want to be too small

(i.e. the resistance too high) otherwise the power dissipated in it will depart too seriously from the maximum possible. A useful, simple rule is to realise that the total percentage harmonic distortion will be less than 10% if the maximum departure from equality of the intercepts referred to does not exceed 10 : 11.

Having determined the best load resistance value, the operating bias can be determined as being at the point X , where X is the mid-point of the load line such that $DX=XB$. If a fuller investigation is then required, the dynamic mutual characteristic $I_A - V_G$, with the appropriate anode load, should be drawn to establish that this operating grid bias is midway between $V_G=0$ and the value of V_G at which this $I_A - V_G$ characteristic commences to bend.

An examination of the most suitable anode loads for power pentodes and beam tetrodes in accordance with these conceptions indicates that, for maximum undistorted power output, the anode load needs to be $\frac{1}{8}$ th to $\frac{1}{18}$ th of the valve A.C. resistance.

Anode Efficiency. Defined as the ratio

$$\frac{\text{alternating power output}}{\text{D.C. power input}}$$

For example, consider the case of a class A amplifier operated for maximum power output, disregarding distortion. It has been shown (p. 147) that then $R_L=R_A$. Obviously the anode efficiency will be 50%.

This can be proved in an alternative manner. Suppose a class A amplifier operates with steady anode voltage V_A and anode current I_A . Then the D.C. power input is $V_A \cdot I_A$. The maximum positive to negative peak excursion that the anode voltage can execute by virtue of an alternating input to the grid will be from V_A to zero, and to a positive maximum of $2V_A$. Correspondingly the maximum possible anode current excursion will be $2I_A$. But the R.M.S. value of the alternating anode voltage will then be $V_A/\sqrt{2}$, and for the current $I_A/\sqrt{2}$. Consequently the alternating power output is $\frac{V_A \cdot I_A}{\sqrt{2} \cdot \sqrt{2}} = \frac{1}{2} V_A I_A$, and the anode efficiency is 50%.

Class B Amplification. A maximum possible efficiency of 50% is a limitation to the power handling capabilities of a valve, especially in the case of radio transmitters where, with apparatus of restricted size, it is required to supply the aerial with as much

energy as possible. For this reason class B and class C amplification practices have been developed. These involve using the valve with a steady, operating grid bias at, or beyond, cut-off.

Such practice is inadmissible in cases where a single valve is used

with a resistance as anode load, since the negative half-cycle of the input does not then produce any corresponding anode current change: rectification is involved. However, if the anode load is an oscillatory rejector circuit, then the introduction of such distortion is not of importance. Fortunately such anode loads are those most useful in R.F. power amplifier practice.

Though the anode current variations of such amplifiers have wave-forms which are rectified and distorted replicas of the input wave-form to the grid, yet such distortion necessarily corresponds to the introduction of second and higher order harmonics (see p. 69), whereas the rejector circuit anode load will only respond to the fundamental. The deliberately introduced distortion is, therefore, of no consequence as regards the ultimate output wave-form. Again, if the distortion introduced is predominantly second harmonic distortion, as in the case of a class B operated triode, then a class B push-pull amplifier, which eliminates even harmonic distortion, is valid (see p. 154), though the anode load is a resistance.

is approximately doubled, in the class B case (fixed bias at cut-off) compared with the class A case, then the fundamental component of the rectified output is capable of supplying the same power to a rejector circuit as would be supplied by a class A amplifier.

The anode efficiency of the class B amplifier is, however, greater because there is a smaller demand on the H.T. supply than when class A working operates. This is because anode current only flows when the alternating grid input is positive, and not when it is negative.

From the analysis given on p. 71, the average value of anode current during one-half cycle is seen to be $2I/\pi$, where I is the peak current. But during every alternate half-cycle the current is zero. Therefore the average current drain on the H.T. supply in class B working is I/π . In class A working, the mean D.C. anode current is $I/2$. Hence class B working demands an average current supply which is only $2/\pi$ of that in class A practice. Consequently a class B amplifier is $\pi/2$ times as efficient, giving a maximum possible efficiency of $\pi/2 \times 50\% = 78\%$.

Class C Amplification. The operating fixed negative bias can be made greater than cut-off, still further restricting the fraction of the input cycle time during which anode current flows. Thus in class C working, the grid bias is as much as twice cut-off value, giving anode current pulses for less than one-third of the operating time, with a consequent anode efficiency of as much as 85%. The considerable second and third harmonic distortion introduced restricts the use of such amplifier practice to solely those cases in which a rejector circuit is used as anode load. Push-pull working is now inadmissible, owing to the odd harmonics involved.

R.F. Power Amplification. To amplify the output of an oscillator, as in the usual radio transmitter master-oscillator, power amplifier system, a class C amplifier is commonly used. Apparatus with a total power output in excess of 250 W. commonly makes use of triode valves, but pentodes are frequently encountered in smaller gear.

To ensure the maximum anode efficiency, the alternating voltage applied to the grid (grid drive) is made great enough to produce a positive grid at the positive peak grid input volts. Thus the input circuit to the amplifier needs to be able to supply a moderate amount of power. When the grid is most positive, the

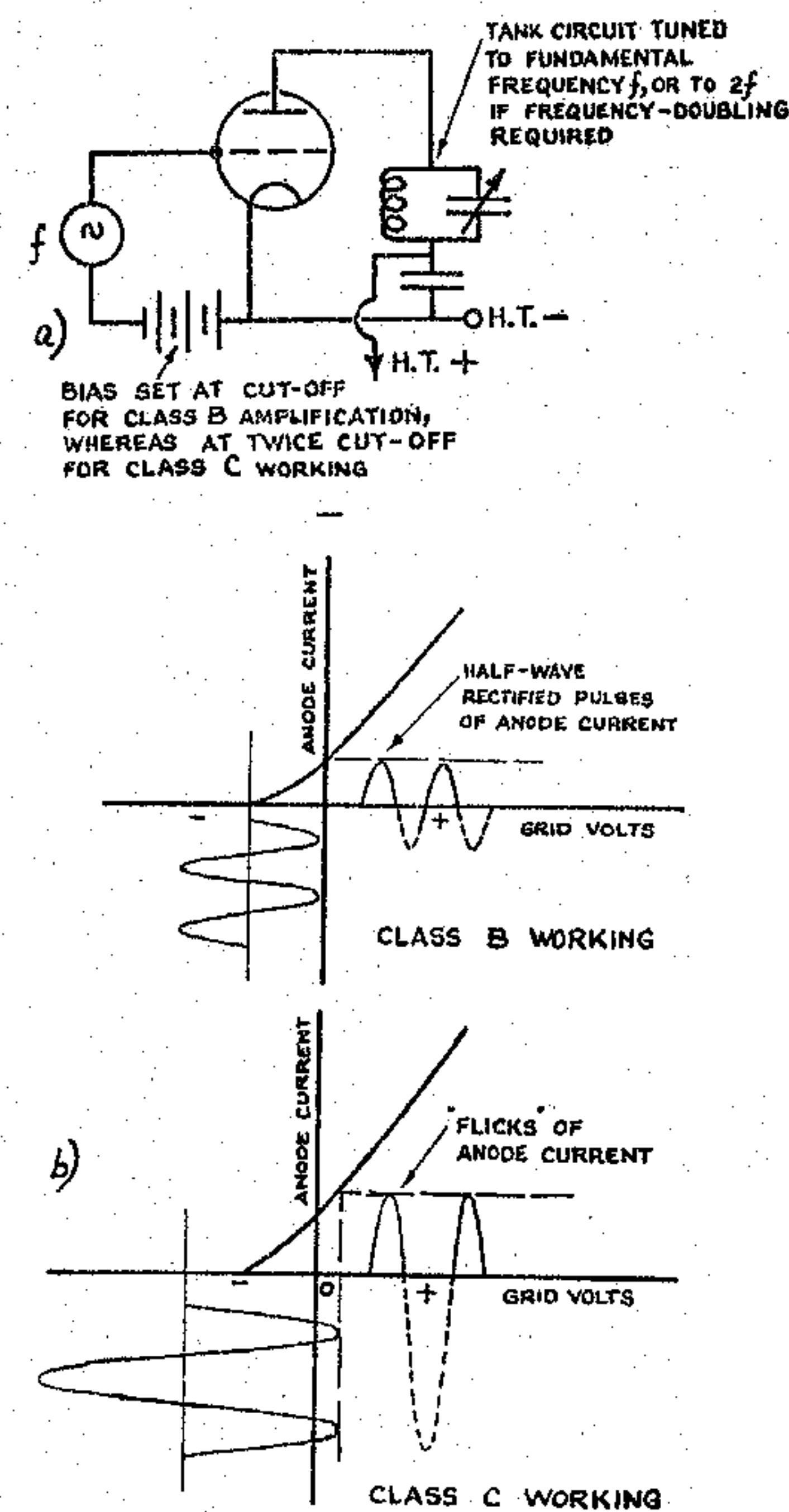


FIG. 63. Class B and Class C Amplification.

From the analysis given on p. 71, it is seen that the wave-form in the case of half-wave rectification possesses a first harmonic component of which the peak value is approximately half the maximum voltage attained. Hence, if the grid alternating input

valve anode current will be large, and the alternating voltage across the tuned circuit anode load will be at its maximum. Since the anode voltage alternates in anti-phase to the grid drive volts (see p. 119), the maximum positive grid voltage will occur simultaneously with the minimum possible anode potential, so that overheating of the anode due to the large current flicks brought about by driving the grid positive is not excessive.

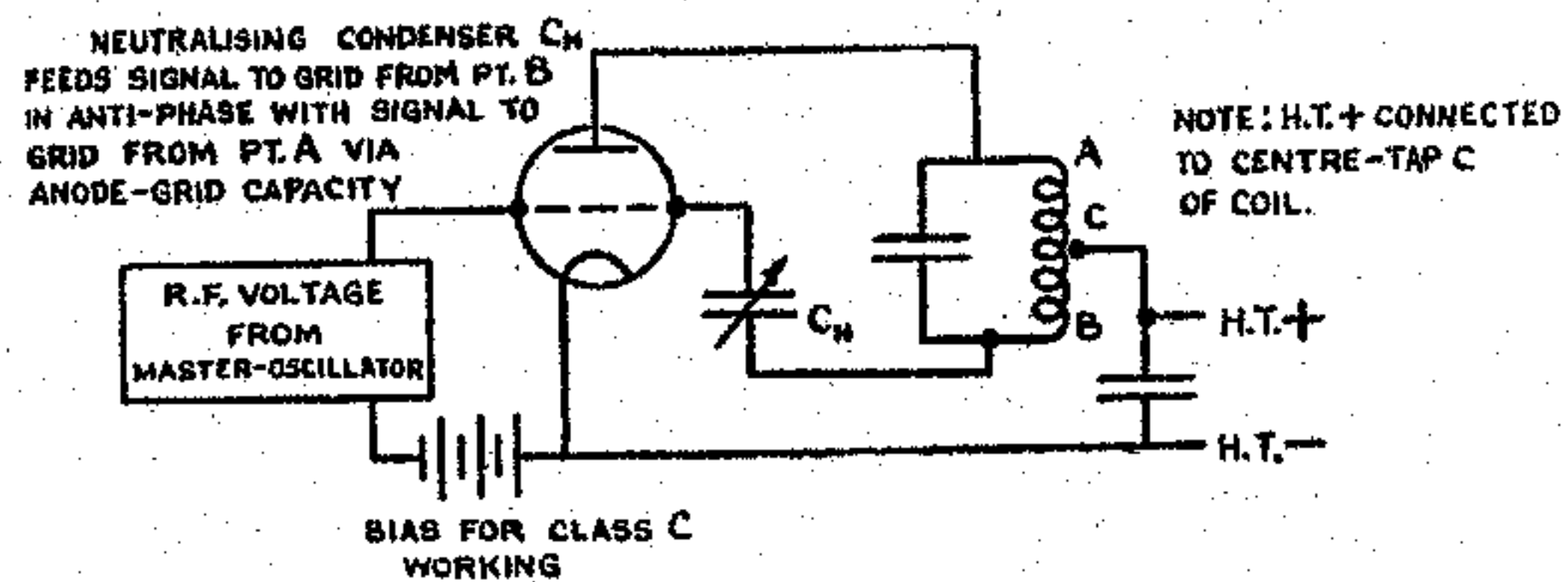


Fig. 64. R.F. Power Amplifier Circuit.

Such R.F. power amplifier circuits need neutralising, as is indicated in fig. 64, to prevent the power amplifier from going into oscillation due to feedback via the anode-grid capacity from the anode tuned circuit to the grid input tuned circuit.

Push-pull Amplification. A circuit arrangement which eliminates distortion at the second and other even harmonics which may be introduced by the valve characteristic, in which a pair of valves is used, generally as a power amplifier, where the grid inputs to the two valves are equal in magnitude, but differ in phase by 180° .

Suppose an A.C. input of sinusoidal wave-form is applied at the primary of the input transformer (fig. 65). Since the centre-tap of the secondary of this transformer is connected to fixed bias battery, voltage V_G , so the grid of valve V_1 will have potentials decided by $-V_G$ plus the alternating voltage across half-secondary A_1C_1 , whereas V_2 grid will vary in accordance with $-V_G$ plus the half-secondary voltage across B_1C_1 . But the potential at point A_1 will be positive with respect to C_1 when the potential of B_1 is negative to the same extent. Therefore the grids of V_1 and V_2 will have potentials varying in anti-phase.

A decrease of the negative potential on V_1 grid will cause the anode current of V_1 to rise, giving a rise of potential across the half-primary of the output transformer C_2A_2 , which is the anode-load presented to V_1 . The potential of point A_2 must therefore

decrease, since the potential of the centre point C_2 is constant at H.T. potential. This action will necessarily be accompanied by a

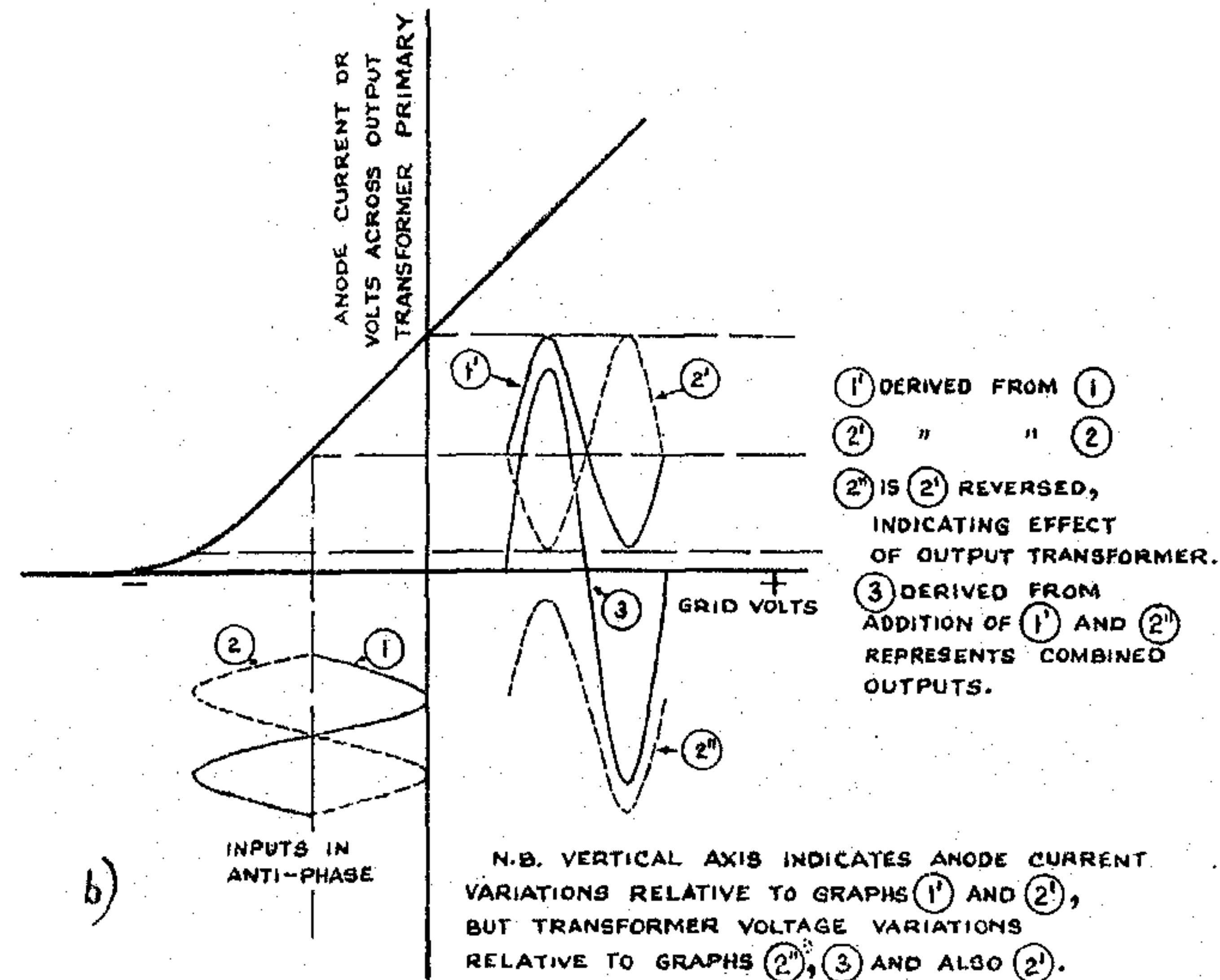
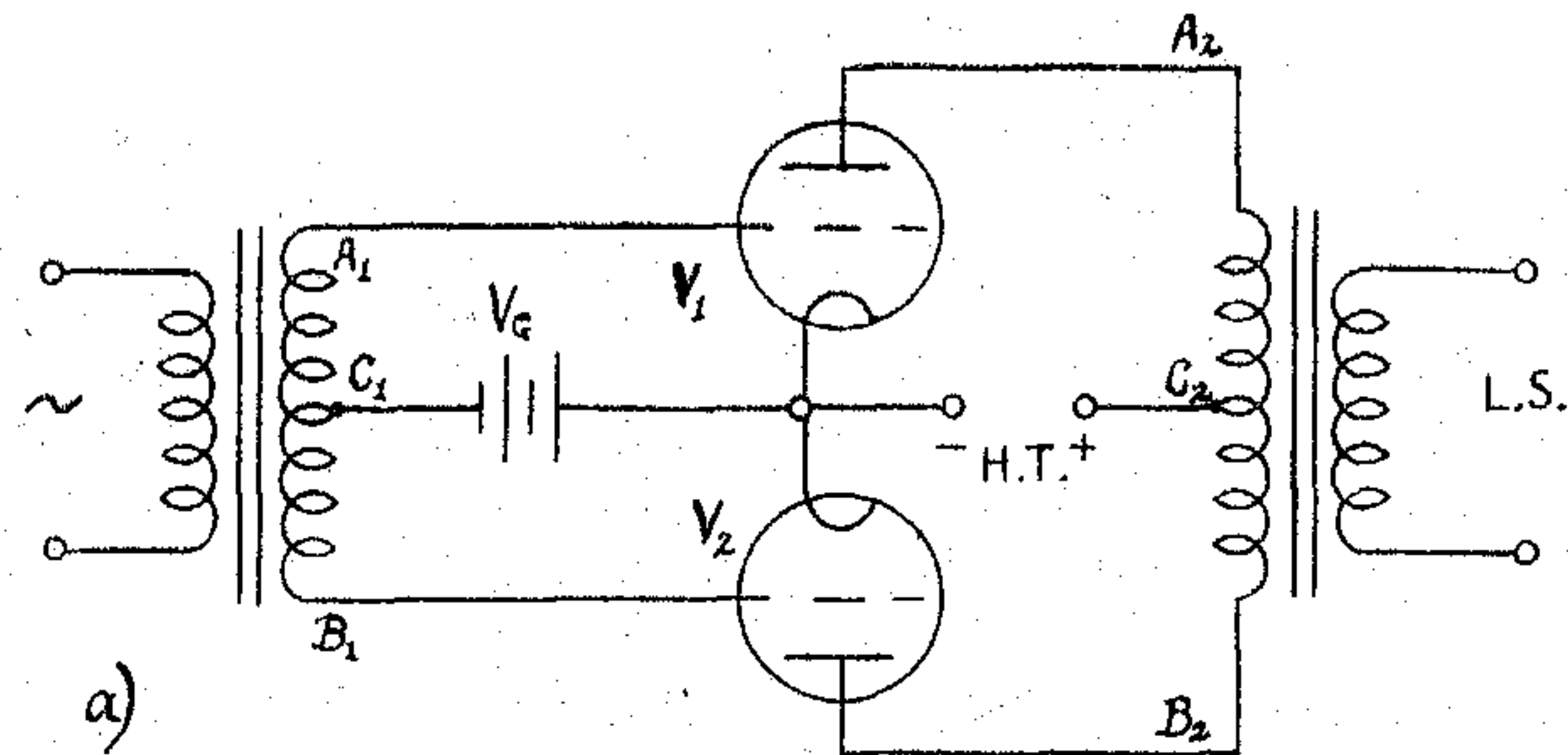


Fig. 65. a, Push-pull Circuit. b, Graphical Illustration of Push-pull Action.

corresponding increase of the negative potential of V_2 grid, producing a fall of the anode current of V_2 . The voltage across the half-primary C_2B_2 of the output transformer must consequently decrease, implying an increase of the potential at point B_2 , since

the potential of centre-tap C_2 is fixed. The total potential variation across the whole of the output transformer primary A_2B_2 is then double the potential variation across either half, A_2C_2 or B_2C_2 , since A_2 potential rises with respect to C_2 to the same extent to which B_2 falls. Hence the two valve outputs are effectively combined across the primary, giving a double output across the secondary, which is connected to a resistive load, such as a loudspeaker.

The D.C. components of the valve anode currents through the output transformer primary are in opposite directions, so the nett D.C. magnetisation of the transformer core is practically zero. The effect of D.C. magnetic saturation of the transformer core causing distortion is therefore eliminated.

A second, and more important, advantage of the push-pull technique is that second and other even harmonic distortion, due to lack of linearity of the valve characteristic over the operating region, is eliminated. Since triode valves produce distortion due to characteristic curvature which is almost exclusively at the second harmonic, so the grid bias may be set at the bend, or even at the valve cut-off region, giving class B working conditions with improved efficiency, and little distortion (see p. 151).

That even harmonic distortion is reduced to zero may be realised on considering a simple mathematical analysis of push-pull action. Suppose the relation between the valve anode-current I_A and the grid potential E_G is given by the general relationship

$$I_A = A + BE_G + CE_G^2 + DE_G^3, \text{ etc.} \quad (183)$$

The alternating grid potential on one valve will be of the form $V_0 \sin \omega t$, whilst that on the other valve will be represented by the anti-phase voltage, $-V_0 \sin \omega t$, V_0 being the peak potential across half the input transformer secondary, $\omega/2\pi$ being the frequency of the input voltage.

Hence for valve V_1

$$I_A = A + B(V_0 \sin \omega t) + C(V_0 \sin \omega t)^2 + D(V_0 \sin \omega t)^3 + \text{etc.} \quad (184)$$

and for valve V_2 , which must have exactly the same shape characteristic,

$$-I_A = A + B(-V_0 \sin \omega t) + C(-V_0 \sin \omega t)^2 + D(-V_0 \sin \omega t)^3 + \text{etc.} \quad (185)$$

Note I_A is written with negative sign here, since it is varying in opposition to the current from valve V_1 .

The combined output across the output transformer primary is $2I_A Z$, where Z is the primary impedance, and $2I_A$ is given by subtracting equation (185) from equation (184).

$$\therefore 2I_A = 2BV_0 \sin \omega t + 2C(V_0 \sin \omega t)^3 + 2E(V_0 \sin \omega t)^5 + \text{etc.}$$

Note that the squared terms, and other terms raised to an even power, vanish in this expression which determines the effective output, since $(-V_0 \sin \omega t)^2 = V_0^2 \sin^2 \omega t$. Moreover,

$$V_0^2 \sin^2 \omega t = V_0^2 \left(\frac{1 + \cos 2\omega t}{2} \right),$$

corresponding to a current component at the second harmonic of the input signal frequency. It is seen that such second, and other even harmonic distortion introduced by the curvature of the valve $I_A - V_G$ characteristics, are therefore eliminated.

It is noteworthy, however, that the percentage of third and other odd harmonic distortions remains the same as if a single valve were used. Since such third harmonic distortion is not noticeably introduced by triode valves, this push-pull method lends itself admirably to the design of receiver and other amplifier push-pull output stages where freedom from distortion is essential. Pentode valves, however, are prone to third harmonic distortion, and should therefore be used with caution in a low-frequency power amplifier push-pull arrangement.

Application of Feed-back to an Amplifier. If a fraction of the output voltage from a valve amplifier is fed back to be placed in series with the input circuit, then desirable or undesirable effects can be produced, depending on the phase of the feed-back voltage with respect to the input signal, and the purpose of the amplifier. If the feed-back is so arranged as to be in anti-phase with the initial input to the amplifier, then *negative* feed-back is achieved. A feed-back that is in the same phase as the input gives *positive* feed-back. Negative feed-back is also called "reverse" or "degenerative"; positive feed-back is also known as "regenerative", or "reaction".

If E = input voltage to the amplifier which is combined with a series feed-back voltage βE_0 derived from the output circuit (see fig. 66a), then the actual voltage to the amplifier input is

$$E_G = E \pm \beta E_0 \quad (186)$$

A plus or minus sign is attached to β depending on whether the feed-back is positive or negative.

The nominal gain, m , of the amplifier, is given by

$$m = \frac{\text{output voltage}}{\text{input voltage}} = \frac{E_0}{-E_G} \left(= \frac{\mu R}{R + R_A} \text{ if resistive anode load used} \right) \quad (187)$$

A negative sign precedes E_G , since the anode voltage of an amplifier varies in anti-phase with the input grid voltage (see p. 120).

$$\therefore E_G = \frac{-E_0}{m} \quad (188)$$

Substituting for E_G in (186) from (188)

$$\frac{-E_0}{m} = E \pm \beta E_0$$

$$\therefore E_0(1 \pm m\beta) = -mE$$

$$\therefore E_0 = \frac{-mE}{1 \pm m\beta} \quad (189)$$

The nett gain, including the effects of feed-back, m_f , is given by

$$m_f = \frac{\text{output voltage}}{\text{signal input voltage}} = \frac{E_0}{-E}$$

Therefore from (189) $m_f = \frac{m}{1 \pm m\beta} \quad (190)$

If $m\beta$ is made considerably greater than unity, then (190) becomes

$$m_f = \pm \frac{1}{\beta} \text{ approx.} \quad (191)$$

indicating that the overall gain of the amplifier depends only on the factor β , which is independent of the characteristic of the valve, the effects of valve "noise" and variations in supply voltage, but depends only on the feed-back network. The gain of the amplifier is, however, much reduced by such feed-back.

If $m_f = +1/\beta$, in the case of positive feed-back, then the feed-back voltage is in phase with the input voltage. Such an amplifier is generally unstable, since any increase of the output voltage

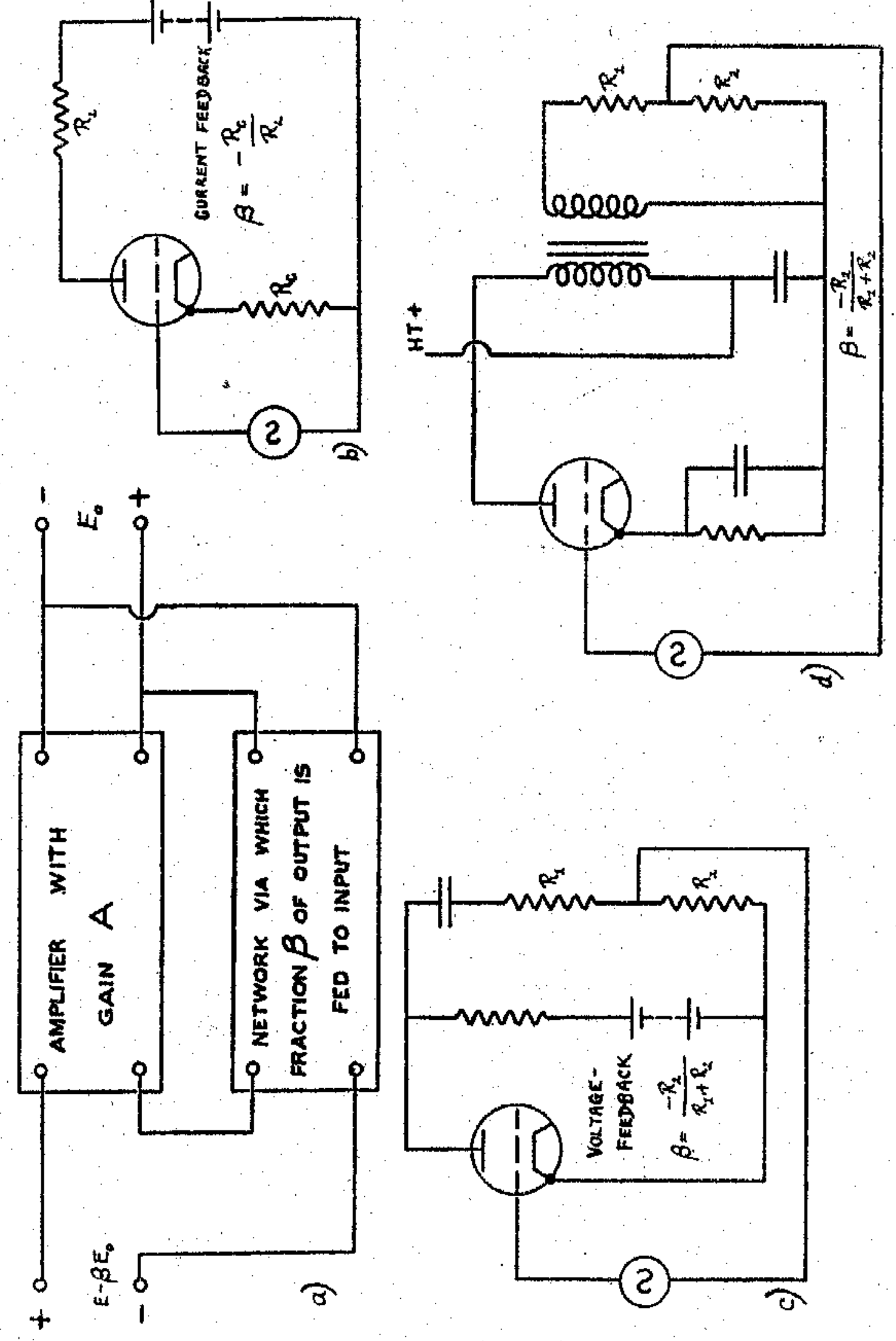


FIG. 66. Negative Feed-back Amplifier Circuits.

causes an increase of the total input signal, causing the output voltage to increase still further, the effect being cumulative.

If $m_f = -1/\beta$, in the case of negative feed-back, then the amplifier is much more stable than is the case of the amplifier without feed-back. This is particularly so the larger the value of $m\beta$, since then the actual input voltage to the amplifier is a small difference between comparatively large signal and feed-back voltages. If the gain m , due to the valve, changes, then the difference between signal and feed-back voltages changes, increasing if m decreases, and vice versa. The actual input voltage therefore changes in such a manner as to compensate for change of the gain m .

$$\text{From equation (189) } \frac{E_0}{E} = \frac{-m}{1-m\beta}$$

The change in gain (E_0/E) caused by a change in amplifier nominal gain m is given by evaluating $\frac{d(E_0/E)}{dm}$.

$$\begin{aligned} \frac{d(E_0/E)}{dm} &= \frac{d[m/(1-m\beta)]}{dm} \\ &= -\left[\frac{(1-m\beta) + m\beta}{(1-m\beta)^2} \right] = \frac{-1}{(1-m\beta)^2} \end{aligned} \quad (192)$$

Hence the change in gain with feed-back for a given change in gain without feed-back is decreased as β is increased negatively, i.e. as the negative feed-back is increased. Vice versa, if β is increased positively, in the case of positive feed-back, then the amplifier stability becomes poorer. This equation (192) indicates also how negative feed-back reduces amplitude distortion, since such distortion results generally from variations of m during the operating time.

The circuits involved in negative feed-back are of (a) the current feed-back type in which the voltage inserted at the input is proportional to the current in the load, (b) the voltage feed-back class where the voltage inserted at the input is proportional to the voltage across the load and (c) current-voltage feed-back in which a combination of (a) and (b) is used. These circuits are illustrated in fig. 66.

Since the gain of these amplifiers is decided by $1/\beta$, in the case where β is a considerable fraction ($m\beta > 10$), and the network

whereby β is achieved may be other than a resistive arrangement, such as a combination of inductance and resistance or capacitance and resistance, so an amplifier of desired frequency-response can be designed, whereas if a resistive feed-back circuit is used, the gain is largely independent of frequency, except for the influence of stray inductance and capacity.

Noise reduction (see p. 164), is brought about in a negative feed-back amplifier. However, this reduction is only for that arising within the valve concerned. Any noise present at the input to the amplifier will be present to the same extent in the output. The reduction of noise as regards that introduced by the amplifier valve itself may be expressed as

$$\frac{\text{Signal to noise ratio with feed-back}}{\text{Signal to noise ratio without feed-back}} = \frac{m_f}{m(1-m\beta)}$$

The Cathode Follower. If a negative feed-back amplifier is used in which the feed-back is obtained by the use of a resistance in the cathode circuit, as in fig. 67a, but the anode load is omitted, the anode being connected directly to the H.T.+ supply, the equation (190) $m_f = m/(1 \pm m\beta)$ is suitably modified by putting $m = \mu R_C / (R_C + R_A)$, where μ and R_A are the constants of the valve used, R_C is the cathode resistance (cf. equation 166) and $\beta = 1$.

$$\therefore m_f = \frac{\mu R_C / (R_A + R_C)}{1 + \mu R_C / (R_A + R_C)} = \frac{\mu R_C}{R_A + (1 + \mu) R_C} \quad (193)$$

The gain of such an amplifier is thus necessarily less than unity. It is therefore used as a current amplifier and not as a voltage amplifier, of which the purpose is to feed the grid with a high impedance input but in which the cathode load can be a low impedance output, yet without serious loss of voltage.

From equation (193),

$$I_A = \frac{\mu E_G}{R_A + R_C(\mu + 1)} \quad (194)$$

where E_G is the alternating grid input, and I_A the alternating anode current, R.M.S. values.

Dividing numerator and denominator of this expression by $(\mu + 1)$ gives

$$I_A = \frac{[\mu/(\mu + 1)] E_G}{R_A/(\mu + 1) + R_C} \quad (195)$$

By comparison with the circuit of fig. 49c, it can be seen that this cathode-coupled stage corresponds to a normal amplifier in which the amplification factor of the valve μ is reduced to $\mu/(\mu+1)$, and the A.C. resistance R_A is lowered to $R_A/(\mu+1)$, the equivalent circuit becoming that shown in fig. 67b.

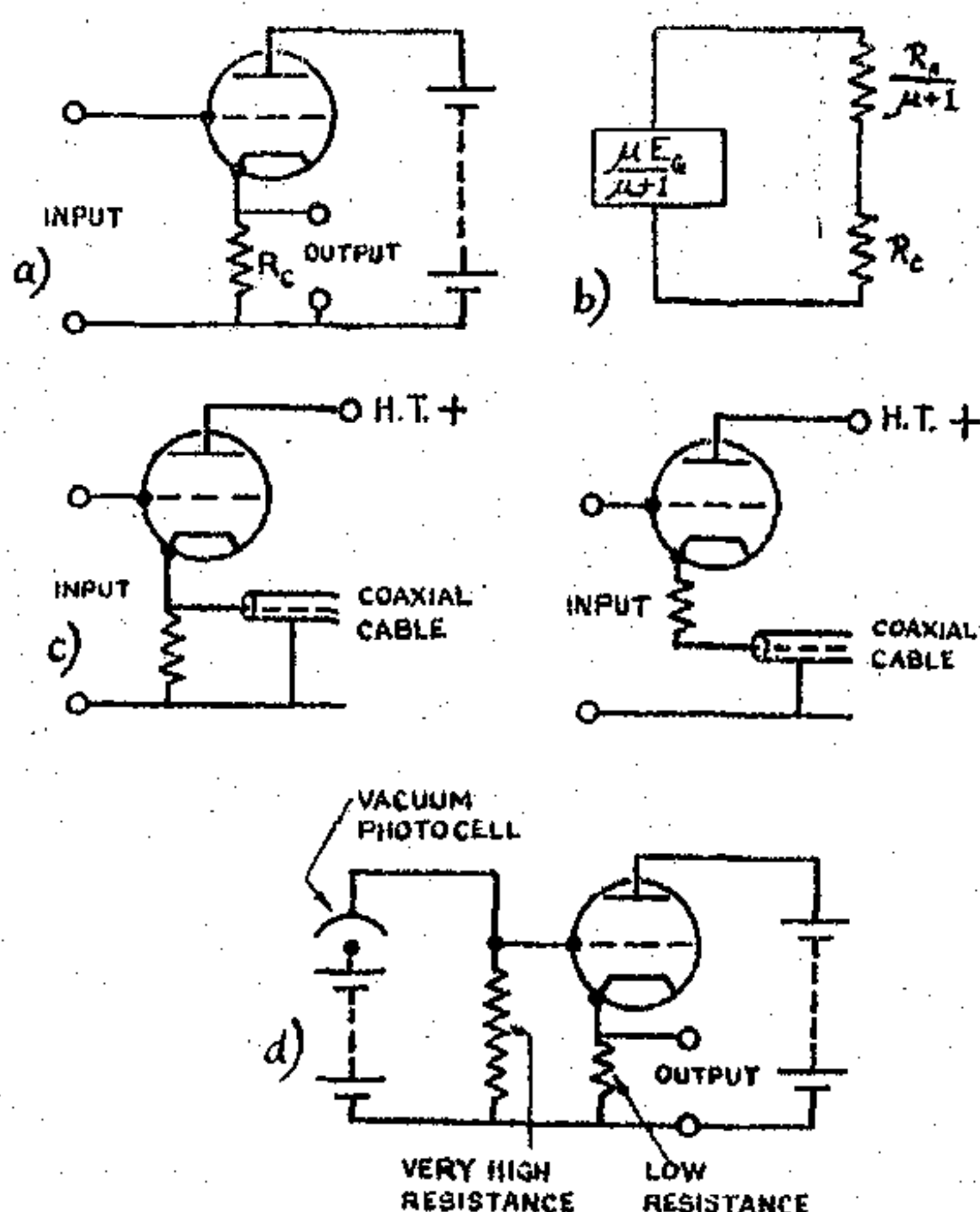


FIG. 67. a, The Cathode Follower. b, Equivalent Circuit for Cathode Follower. c, Cathode Follower used to couple to Transmission Line, d, Cathode Follower as D.C. amplifier.

The output resistance R_0 is effectively the valve resistance and R_C in parallel, and equals

$$\frac{R_C [R_A/(\mu+1)]}{R_C + R_A/(\mu+1)} = \frac{R_C R_A}{R_A + R_C(\mu+1)}$$

which in the case of a pentode,* where $\mu \gg 1$, becomes

$$R_0 = \frac{R_C}{1 + R_C g_m} \tag{196}$$

on employing the relationship $g_m = \mu/R_A$. For example, in the

* In using a pentode in a cathode-follower circuit, the screen must be kept at constant potential with respect to the cathode.

case of a pentode, suppose $\mu=1000$, $R_A=250 \text{ k}\Omega$, $R_C=1000 \Omega$, and $g_m=4 \text{ mA/V}=0.004 \text{ ohms}$, then

$$R_0 = \frac{R_C}{1 + 1000 \times 0.004} = \frac{1000}{5} = 200 \Omega.$$

$$\text{and the gain} = \frac{\mu R_C}{R_A + R_C(\mu+1)} = \frac{1000 \times 1000}{250,000 + 1000(1001)} = 0.8.$$

This low impedance output, one side of which is at earth potential, makes such circuits eminently suitable for coupling the output of an oscillator to a transmission line or aerial circuit in a transmitter, where a careful match is required between the output circuit and the load (see fig. 67c). Moreover, because of the low output impedance, the output voltage has good regulation where the input to the cathode-follower stage may have poor regulation. Another advantage of this circuit is that there is no polarity inversion: the output voltage variation is in phase with the input alternating voltage.

The cathode follower circuit also exhibits reduced Miller effect (cf. p. 134), the effective input capacity being reduced in accordance with the relationship

$$\begin{aligned} &\text{Equivalent input capacity} \\ &= \text{actual input capacity } (C_{CC}) \times \left(1 - \frac{E_0}{E_G}\right). \end{aligned}$$

A cathode follower may be used with advantage in photoelectric cell amplifiers, since this circuit technique enables the grid resistance across the input to be very high, yet with a low output cathode resistance. Thus using ordinary valve types, the presence of positive ion current and grid emission prohibits the effective use of an input resistance greater than 2 M Ω . (see p. 119). Suppose the photocell current is 0.05 μA ., then a D.C. voltage input to the amplifier of $0.05 \times 2 = 0.10 \text{ V}$. is achieved on switching on the cell illumination. If the D.C. amplifier is normal (fig. 48) then a voltage gain of 100 times, and so an output of 10 V. is easily obtained. Compare the use of a cathode-follower amplifier. Even using normal triode and pentode valve types, the input resistance can now be as much as 100 M Ω ., giving an effective input voltage of $0.05 \times 100 = 5 \text{ V}$. If a gain of 0.8 is realised, then the output voltage across, say, a 5 k Ω . cathode load will be 4 V. It would

seem as though the cathode technique was thus only 40% as effective as the provision of the ordinary D.C. amplifier. In practice, however, great benefit is obtained from the use of the cathode-follower because it is virtually insensible to the supply voltage fluctuations and circuit variations which make normal D.C. amplifier practice so tedious and unreliable.

“Noise” in Amplifiers. It would seem that a consideration of the methods of coupling both A.C. and D.C. amplifiers in cascade would lead to the belief that there was no limit to the total amplification possible: it was simply a matter of ensuring constant voltage supplies and using a sufficient number of valve stages coupled together to obtain amplifications of several million. In practice this is not so: a limit is set by the “noise” which arises in the amplifier, due to minute random fluctuations of the current. These are particularly obnoxious in the first stage, since it is there that the true signal is small, and the “noise” becomes of comparable magnitude, giving a signal to “noise” ratio which is sufficiently small to make the eventual output unintelligible.

This “noise” arises in two places:

(a) Thermal agitation noise, or Johnson noise, brought about by fluctuations of the current in ordinary electrical conductors due to the thermal agitation of the conducting particles. In this connection the input resistance to the first amplifier is usually the only one which need be of concern, because it is only there that the signal current is sufficiently small for the “noise” current to be of comparable magnitude.

An electric current is due to the motion of electrons through conducting material, and the current due to an applied signal voltage is combined with the small currents due to the thermal agitation of the electrons. During any long period of time the nett effect of these thermal currents is zero. At any given instant, however, this is not the case—there may be a slight preponderance of random electron motion in one direction over that in the other. Such transient currents are of very complex wave-form, and produce voltages across the resistance of which the harmonic components extend over a very wide frequency band.

An expression for thermal “noise” is

$$E_N^2 = 4kT \int_{f_1}^{f_2} Rdf. \quad (197)$$

Due to Nyquist,* this equation gives E_N , the R.M.S. value of the E.M.F. produced in series with the resistance of the conductor R , where k is Boltzmann’s constant, T is the absolute temperature, f is the frequency and R is the actual or equivalent shunt resistance of the circuit, being L/CR in the case of a rejector circuit.

Integrating this equation over the frequency range (f_1-f_2) gives

$$E_N = \sqrt{4kTR(f_1-f_2)}. \quad (198)$$

Substituting for k , then at normal room temperatures

$$E_N = 1.25 \times 10^{-10} \sqrt{R(f_1-f_2)}. \quad (199)$$

An immediate partial remedy to the elimination of this noise voltage is to restrict the band width (f_1-f_2) which the amplifier passes. If $R=100 \text{ k}\Omega$, and $(f_1-f_2)=10 \text{ kc./s.}$, then substitution in (199) gives

$$E_N = 1.25 \times 10^{-10} \sqrt{(10^5 \times 10^4)} = 4 \mu V. \text{ approx.}$$

(b) Shot or “schrot” noise. First investigated by Schottky,† is due to a comparable fluctuation of the current in valves due to the random emission of individual electrons. Thus the anode current of a valve is constant considered over any finite time interval, but at a particular instant the number of electrons arriving may be slightly different from the number at another instant, though the average number is constant. In other words, “shot noise” is due to the finite magnitude of the electron charge motions which constitute an electric current, where the number of electrons flowing per second will be constant, but where the number per microsecond will fluctuate slightly about the mean value.

Added to this inevitable cause of current variation, there is a second source of fluctuation which is decided by the physical nature of the emitting cathode surface. This is called “flicker effect”, and is particularly prevalent if the cathode surface is not smooth, but pitted with minute holes which occasionally release bursts of electrons. Added to this there are noise effects due to ionisation of the residual gas in the valve and due to secondary emission from the valve electrodes.

Shot noise, considered as separate from flicker effect, etc., can be expressed by the equation

$$I_N^2 = 2I_A e(f_1 - f_2) \quad (200)$$

in the case of a saturated diode, where I_A is the anode current, and I_N is the R.M.S. value of the variation of I_A .

In the case of non-saturated triode and multi-electrode valves, the effect is reduced by the presence of space-charge, which acts as a cushion, or reservoir of electrons. Thus valves in which the space-charge effect is high are preferable for reduction of shot noise. In these cases, the effect of total noise is stated as the equivalent resistance which would give the same noise voltage due to thermal effects, and the magnitude of this resistance is proportional to I_A/g_m^2 . Hence a valve of large mutual conductance g_m for a given anode current I_A , is necessary for low noise levels.

The triode valves are most free from this noise defect. The pentode has an equivalent shot noise resistance about five times that for the corresponding beam tetrode. This is because the beam tetrode has low screen current, high space-charge effect between beam plates and low secondary emission. Frequency-changer valves (see p. 210) are bad because their conversion conductances are low, and they also produce noise by virtue of their oscillator section. Thus it is preferable to use an R.F. beam tetrode amplifier before the frequency-changer in a super-heterodyne receiver if a particularly high signal/noise ratio is required.

A minimum signal/noise ratio of 5 to 6, or some 15 db.* is desirable in amplifier and receiver practice, where the noise concerned is the total noise brought about by the above effects.

Supply Voltage Regulation. If electronic circuits, such as amplifiers, are used in any kind of measuring or indicating device where a constant output reading is required from day to day for the same input conditions, then it becomes essential to pay considerable attention to the question of the supply of constant valve filament and anode voltages. This is particularly the case where the H.T. and L.T. supplies depend ultimately on the A.C. or D.C. mains, as in power-pack practice.

* Decibels = db. = $10 \log_{10} (P_1/P_2)$, where P_1 and P_2 are two powers,
 $= 20 \log_{10} (V_1/V_2)$, where V_1 and V_2 are two voltages.
 $\therefore 15 \text{ db.} = 20 \log_{10} (V_1/V_2) \quad \therefore V_1/V_2 = \text{antilog}(0.75) = 5.63.$

Apart from manual control of a potentiometer, or variac across the mains, bringing an indicating voltmeter to a constant reading, there are four ways in which stabilisation of a voltage (or current) supply can be arranged. They are (a) by means of a constant-voltage transformer; (b) using a barretter; (c) by gas-filled discharge tube, or stabilovolt; (d) by use of thermionic vacuum tubes. In all these devices an unavoidable difficulty arises in that the voltage (or current) change must occur before it can be compensated; it is a desirable feature of a stabiliser, therefore, that such compensation takes place with as little time-lag as possible. In this connection, and in other ways, the use of thermionic valves as regulating means are the most successful.

(a) Constant voltage transformers employ magnetic saturation to achieve a constant A.C. voltage output. Thus transformers are available with ratings up to 25 kW. which give a secondary voltage constant to within $\pm 1\%$ for variations of primary voltage up to $\pm 15\%$. In such transformers the usual arrangement is for two transformers to be used with their primary windings in series additively, and their secondary windings in series with the load, but so wound that the A.C. voltage outputs are in anti-phase with each other. One of these transformers has an iron core which is partially magnetically saturated over the range of primary voltage required, and gives the larger secondary voltage. When the A.C. voltage applied increases in magnitude the fraction of the total applied to the saturated transformer decreases. Thus the secondary voltages become more nearly equal, it being a matter for the designer to arrange that such change of output compensates exactly for the primary supply change. Frequently the saturated transformer has a condenser connected across its secondary to improve the regulation, and to correct the wave-form. The chief difficulty with such arrangements is that the output wave-form is no longer sinusoidal, and in some circuits the change of wave-shape with change of supply voltage may be as disturbing as a change of voltage would be. Again, if the frequency of the A.C. mains supply varies, then the voltage variations from such transformers are worse than from an ordinary transformer. Transformers are available, however, which are guaranteed to be unconscious of both primary voltage and frequency changes within certain limits.

A constant voltage transformer feeding the primary of an ordinary transformer power pack can regulate the ultimate H.T. supply from such a pack. Again, these transformers can be used for maintaining constant A.C. heater voltages, or lamp filament supplies.

(b) The barretter is somewhat like an ordinary electric lamp of which the filament is iron wire operating in a hydrogen atmosphere. The filament and hydrogen pressure are so adjusted that the current through the lamp is largely independent of the supply voltage. The commonest use of these barretters is in universal A.C.-D.C. mains receivers where a barretter is placed in series with all the valve heaters across the A.C. mains

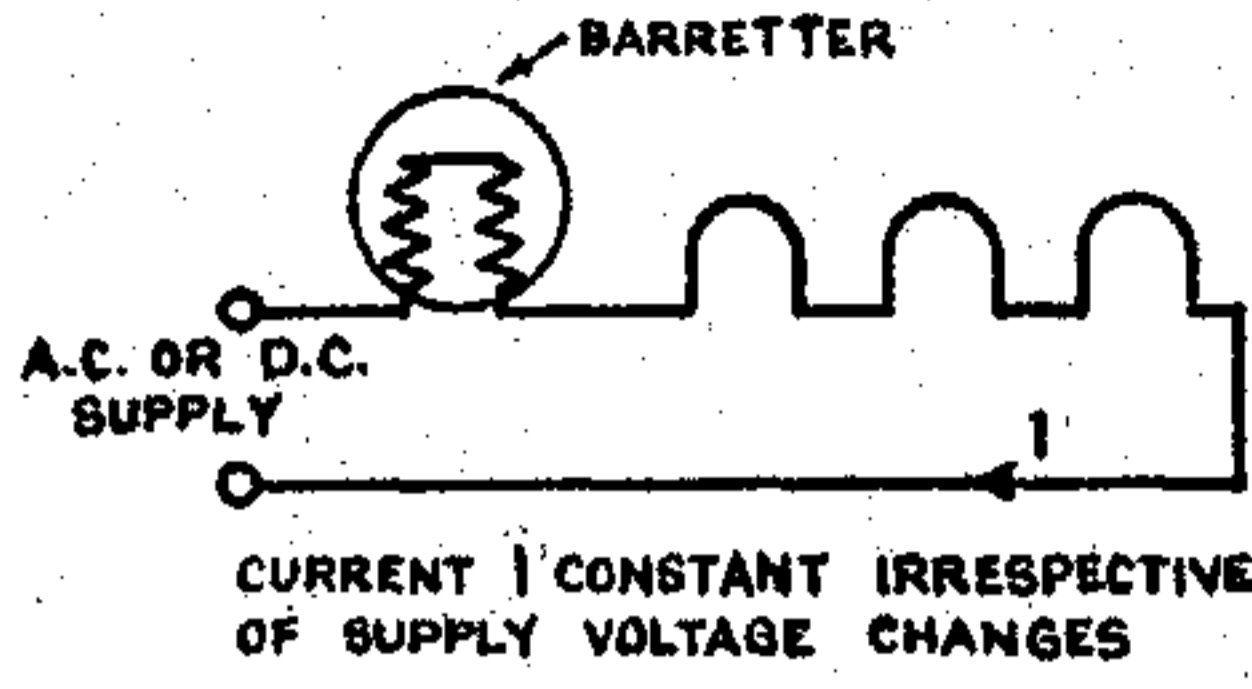


FIG. 68. The Barretter.

supply, fig. 68, barretters being available which have a current capacity equal to the current rating of the 13 V. heaters commonly employed in A.C.-D.C. valves.

The iron filament presents a resistance to the supply E.M.F. which varies in such a manner that the series current is constant. Thus if the supply E.M.F. increases the current will tend to rise. However, such current increase causes greater heating of the filament, and if the filament resistance temperature coefficient is correct, then the increased filament resistance can compensate for the increased supply voltage. This coefficient is arranged to be correctly compensative over a wide range of voltages by the use of iron as the resistance element, in conjunction with the rate of conduction of heat away from the filament depending on the pressure of the surrounding hydrogen atmosphere.

The time lag for compensation to occur is a snag in using this method of stabilising. Again, the glass bulb of the barretter takes more than half an hour to reach an equilibrium temperature. Apart from its great use in providing valve heater currents in universal receivers, the author has found that barretters are of little use in trying to arrange constant current supplies for any purpose where laboratory measurements are to be made.

(c) Gas-discharge tube regulators, such as the neon lamp and the specially prepared stabilovolt, are of considerable value in achieving constant H.T. supplies. This is due to the peculiar

characteristic of the two-electrode tube filled with an inert gas at low pressure whereby, once a glow discharge begins, the voltage across the tube remains nearly constant irrespective of the current through the gas.

The current through the tube increases with voltage until the striking potential is reached. Thereafter the voltage drop across the tube falls to a lower value, and further current increase is accompanied by practically no voltage change. The cathode glows, and as the current is raised, this glow extends to cover the whole cathode area.

The power supply voltage needs to be more than the striking potential. The circuit used is shown in fig. 69a, constant voltage being obtained across the load shown. The series resistance R is necessary to prevent exceeding the tube current rating. $R = (E_s - E_o) / I_m$, where E_s is the total E.M.F., E_o is the load voltage, and I_m the maximum tube current. Any increase of current through the load, due to fall of load resistance, is accompanied by a tendency to greater voltage drop across R . This tends to reduce the voltage across the tube and load, but less current is then taken by the tube, compensating for the increase of load current, so that the tube and load voltage remain constant, because the voltage drop across R remains the same. Again, if the supply voltage increases, the additional current through the regulator tube will be sufficient to make the voltage drop across R compensate for the change, so the load voltage remains the same.

These tubes are especially useful in the form of the stabilovolt in which the cathode is in the form of a number of metal cylindrical electrodes, one inside the other and insulated from one another. With appropriate external resistances, such an arrangement can be used to provide a total constant voltage of some 300 V. or more which can be subdivided into three or four parts as a

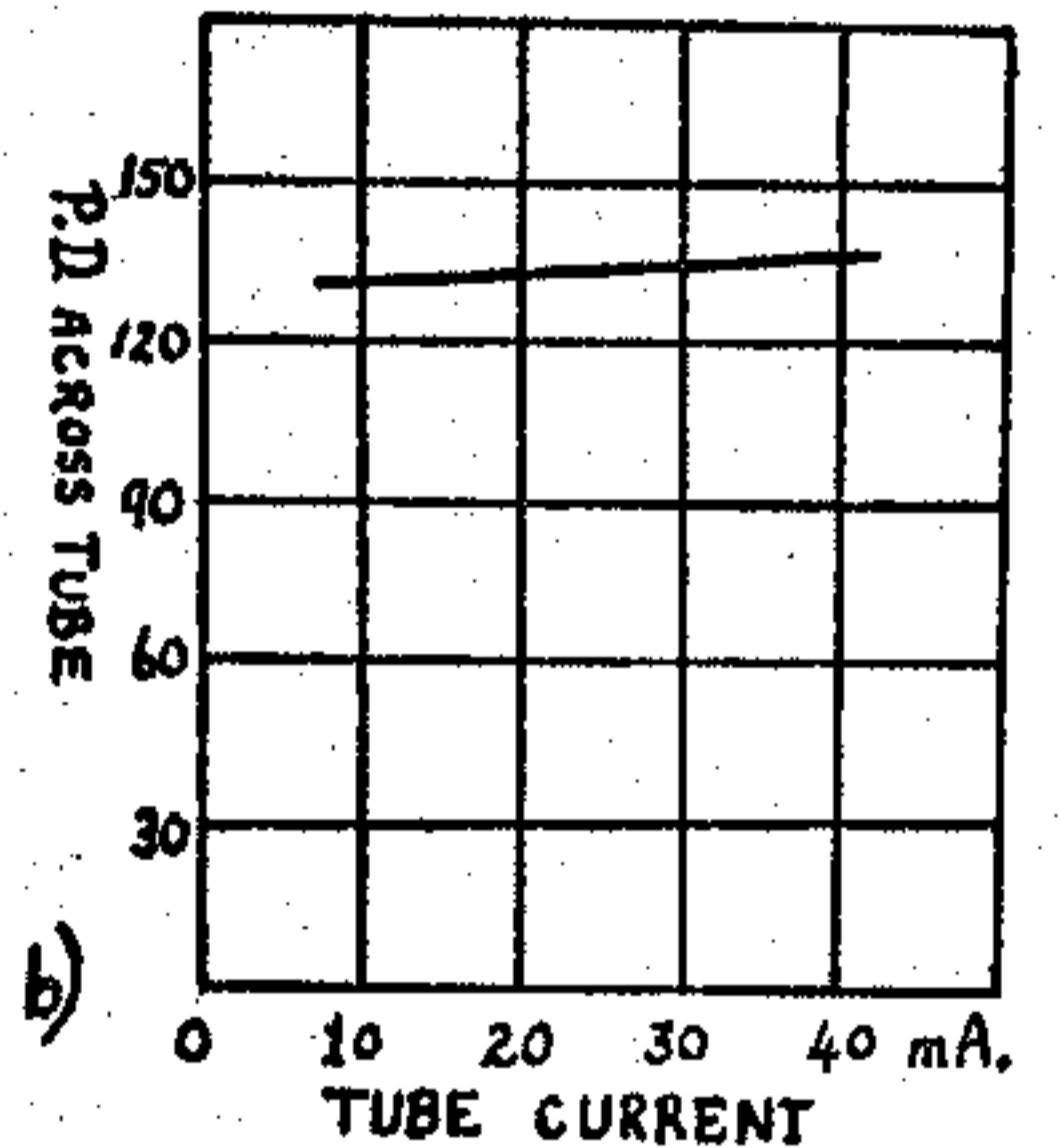
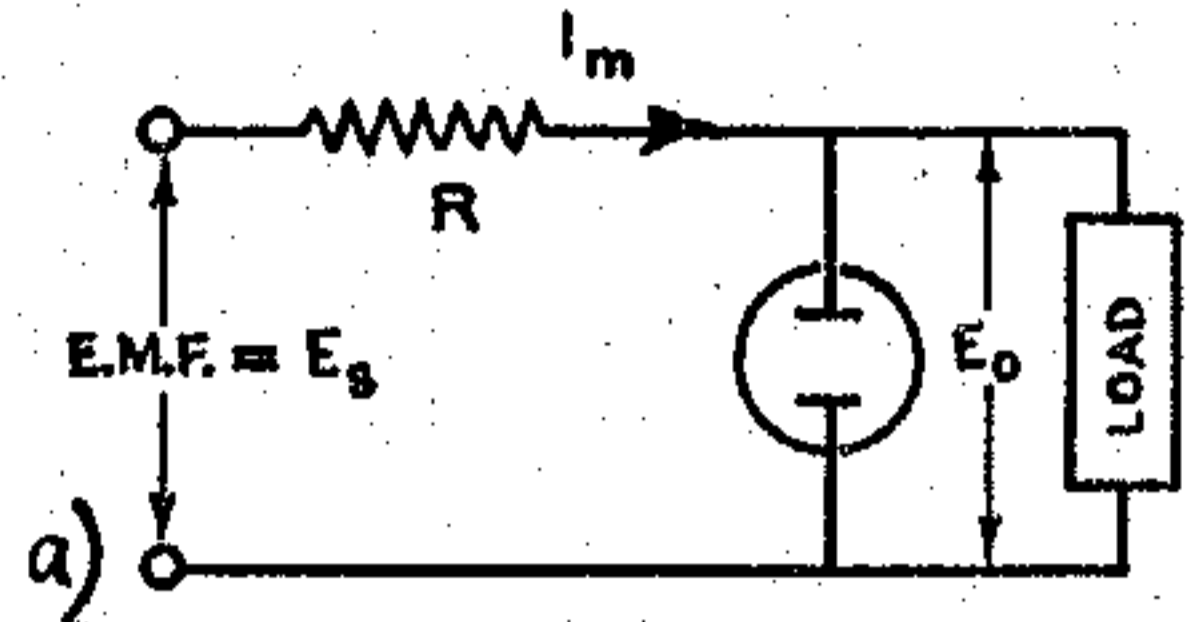


FIG. 69. a, Gas-filled Voltage Regulator. b, Voltage-current Characteristic.

potential divider. The alternative is to use a number of neon tubes, or preferably stabilisers like the Cossor S130, in series with one another.

Electronic Regulators. The best types of voltage and current regulators are those employing valves. Whereas a gas-discharge tube cannot readjust itself in less than 1/10th msec., an electron tube is practically instantaneous in its action. The chief disadvantage associated with the use of valves is in obtaining large current values. Thus a regulated current of 0.5 amp. would either require the use of a large type of power valve, or a number of normal valve types in parallel.

A saturated diode, with its constant anode current above saturation anode potential can be used. However, valves with oxide-coated cathodes do not operate for long under saturation current conditions. The bright emitter tungsten filament could be used, but then the provision of a carefully regulated filament current is a problem.

The basic circuit employed using a triode valve regulator is shown in fig. 70a. If the H.T. supply voltage rises, the voltage across the load tends to rise, and so does the cathode potential of the triode valve in series with the load. With a given bias, obtained as shown, an increase of H.T. is accompanied by a tendency to a positive increase of cathode potential, and as a result an increase of negative grid bias relative to cathode. So the valve current is reduced, and the voltage drop across it rises, which can be made to compensate for the increased supply volts, the load voltage remaining constant if correct working conditions are arranged. The opposite action takes place if a fall of supply voltage occurs. Similarly, any undesirable changes of the load current are regulated. A resistance is inserted in series with the valve grid to prevent excessive grid current flow when the H.T. supply is switched off, and the grid goes positive because of the continued supply from the bias battery. Alternatively, a gas-discharge tube can be used to provide the grid bias, as in fig. 70b.

A mutual-conductance, or g_m -regulator can be arranged as in fig. 70c. Here the H.T. supply E.M.F. to be regulated is placed across a potential divider, R_1 and R_2 in series. Let the total H.T. = E volts, and let E_L = voltage across the load supplied. Suppose E changes by an amount ΔE , where ΔE is positive or negative. Then the change of grid voltage is $R_1 \Delta E / (R_1 + R_2)$.

This bias change will produce a change of anode current through R_3 of $g_m R_1 \Delta E / (R_1 + R_2)$, where g_m = valve dynamic mutual conductance. If this is equal to the change ΔE of the supply E.M.F.,

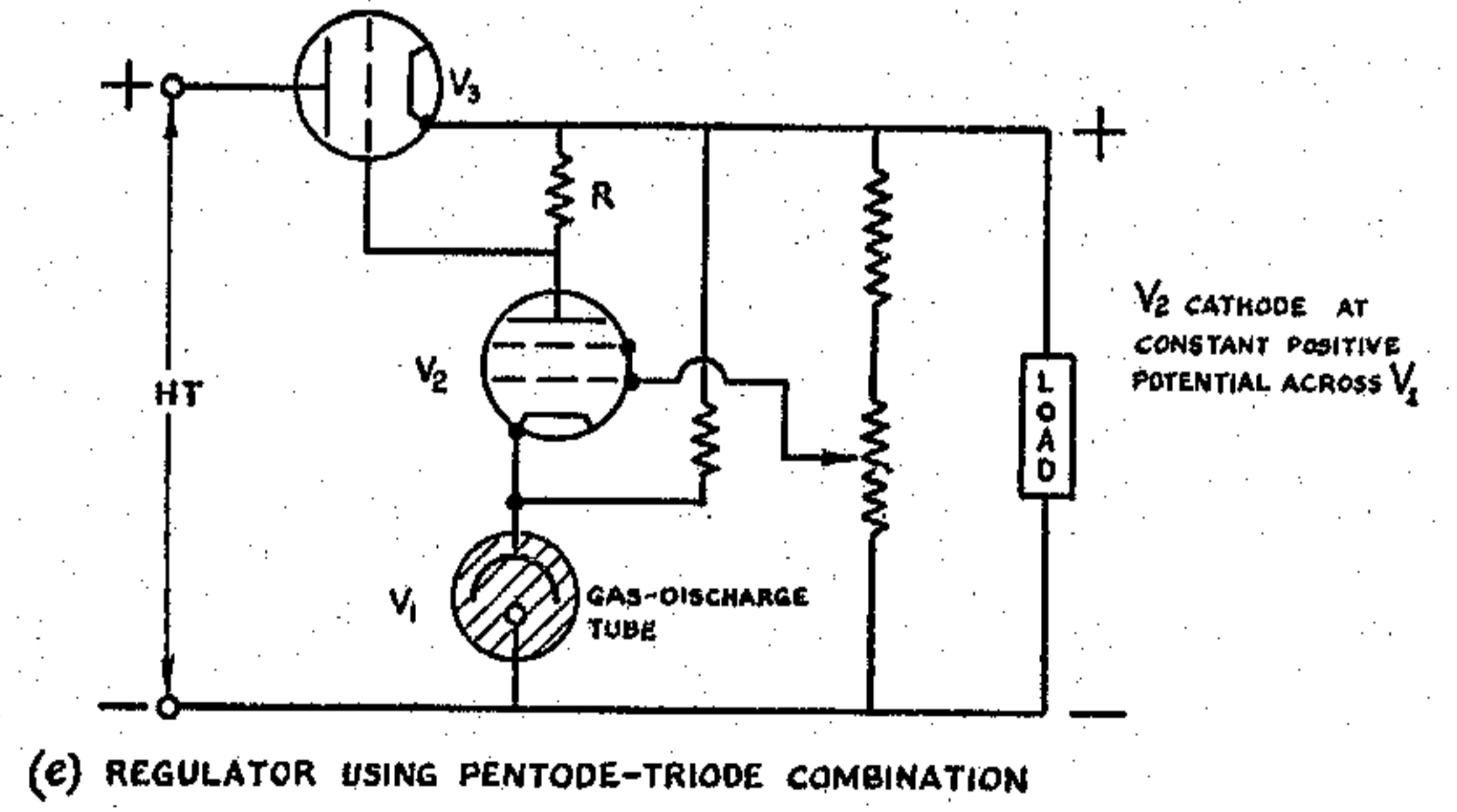
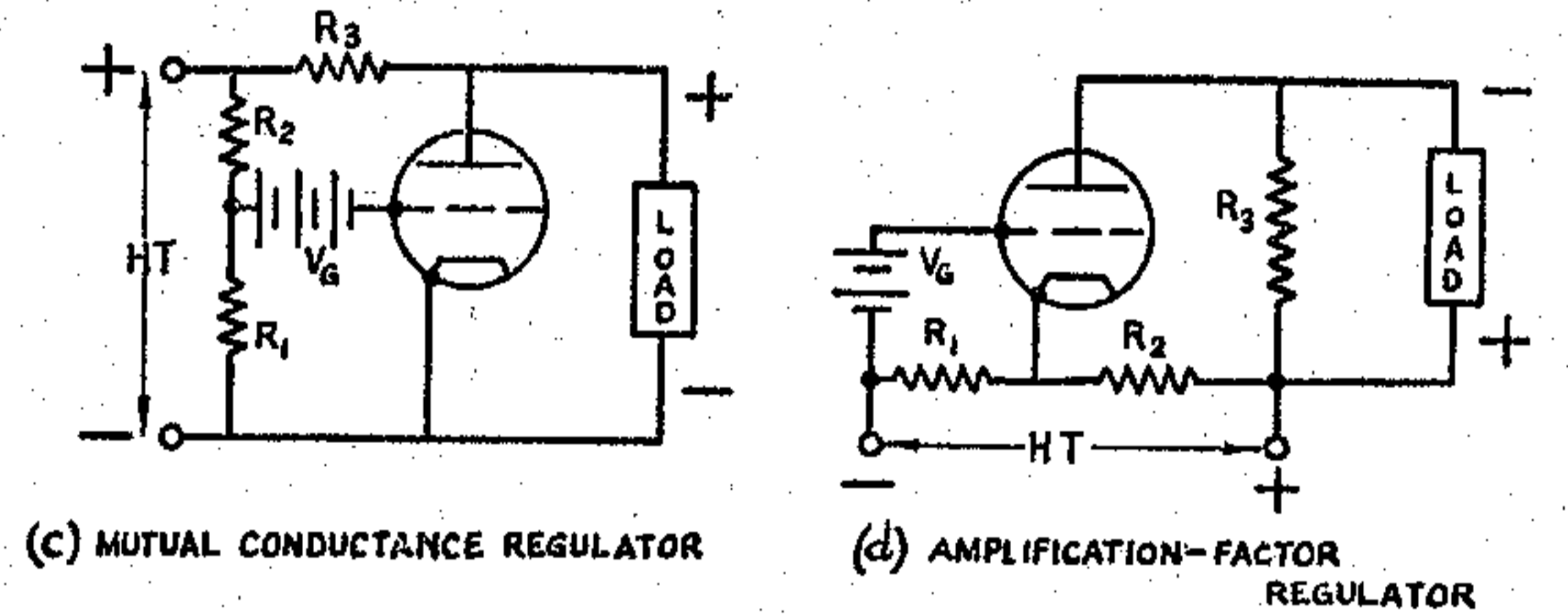
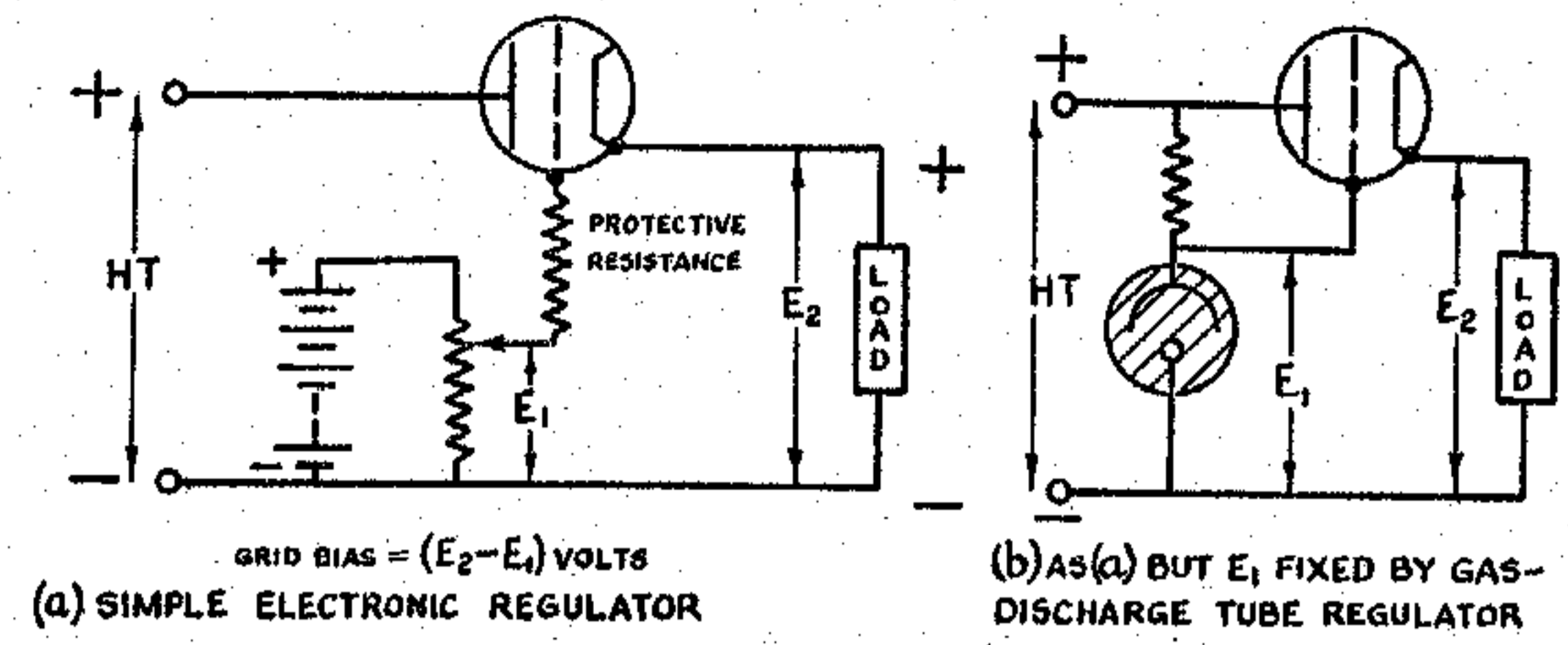


FIG. 70. Electronic Regulator Circuits.

then the anode voltage, and so load voltage, will remain constant, because then an increase of E is accompanied by an equal increase of the P.D. across R_3 , and correspondingly for a decrease of E there is an equal decrease across R_3 , whilst the anode voltage is

equal to the difference between E and the P.D. across R_3 . Hence for effective stabilisation of the load voltage

$$\Delta E = g_m \frac{R_1 R_3}{R_1 + R_2} \cdot \Delta E.$$

$$g_m = \frac{R_1 + R_2}{R_1 R_3}.$$

The actual values of R_1 , R_2 and R_3 chosen will depend on the valve characteristics considered in conjunction with the load E.M.F. and current required. The grid bias relative to the cathode will have a mean value of $[R_1/(R_1 + R_2)E - V_c]$, which decides the value of the bias battery voltage necessary to achieve a suitable negative bias for class A operation of the valve.

An amplification-factor, or μ -regulator, is shown in fig. 70d. Here a change of E by an amount ΔE causes a grid voltage change of $R_1 \Delta E / (R_1 + R_2)$ and an anode voltage change of $R_2 \Delta E / (R_1 + R_2)$. Since the change of grid volts is here necessarily of opposite polarity to the change of anode volts, so the anode current through R_3 , and hence the P.D. across R_3 and the load will remain constant, if the effect on the anode current of the grid voltage change is equal and opposite to the effect on the anode current of the anode voltage change. But in accordance with the definition of amplification-factor, this will be the case if the change of anode voltage divided by the change of grid voltage equals μ . Therefore the circuit is an effective regulator when

$$\frac{R_2 \cdot \Delta E}{R_1 + R_2} \div \frac{R_1 \Delta E}{R_1 + R_2} = \mu.$$

$$\therefore \frac{R_2}{R_1} = \mu.$$

The ratio of R_1 to R_2 is therefore decided. The values of R_1 , R_2 and R_3 will depend on the valve chosen, and the demands of the load. To operate the valve at its usual grid bias for class A working, it is to be noted that the grid potential relative to the cathode is $[V_c - R_1 E / (R_1 + R_2)]$.

Regulators using pentode valves with their constant-current characteristic and high amplification factor are capable of very great control ratio. A typical circuit is shown in fig. 70e. The bias

on V_3 depends on the P.D. across R , which rises negatively if the current through R rises, and decreases if the current through R falls. But the rise and fall of the current through R depends on the grid bias on V_2 , which will change in direction in the same way as any change of load voltage. So a tendency for the load voltage to increase, sensitively controls the increase of negative bias on V_1 , which makes the A.C. resistance of V_3 greater. The P.D. across V_3 therefore rises, which can be made to compensate exactly for any tendency for the load voltage to increase. Vice versa, a tendency for a decrease of load voltage to occur is offset.